


CHUKA UNIVERSITY
SECOND YEAR FIRST SEMESTER EXAMINATIONS FOR BACHELORS OF COMPUTER
SCIENCE

COSC 211: DIGITAL ELECTRONICS

SECTION A (COMPULSORY)

QUESTION 1 (COMPULSORY) [30 MARKS]

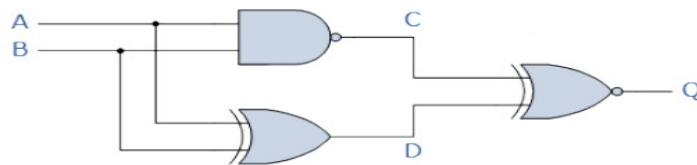- a) Using a circuit diagram, explain the operation of a full subtractor. (6marks)
- b) With the help of a circuit diagram, describe what we mean by a combinational circuit. (4marks)
- c) Below is a circuit. Use it to answer the questions that follow:-



- i) Write the truth table of the circuit above (4marks)
 - ii) From the truth table, can the circuit be minimized? If so draw the minimized circuit. (2marks)
 - iii) Explain a benefit of simplifying digital circuits (1mark)
- d) Outline FOUR differences between digital and analogue electronics (4marks)
 - e) Explain FOUR characteristics of a shift register (4marks)
 - f) Prove that the following equations are the same. (5marks)

$$ABC + A\bar{B} \cdot (\bar{A} \bar{C}) = A(\bar{B} + C)$$

SECTION B (Answer two question from this section)


QUESTION 2 [20 MARKS]

- a) Distinguish between sequential access and direct access methods of storage devices, naming an example in each case. (4marks)

- b) With reference to the following SOP


$$Z = f(A, B, C) = \bar{A}B + B\bar{C} + BC + A\bar{B}\bar{C}$$

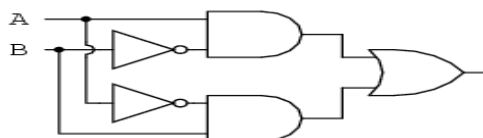- i) Minimize above equation using Karnaugh Map (4marks)
 - ii) Minimize the above equation using Boolean laws (4marks)
 - iii) Write the resultant truth table of the minimised circuit (3marks)
 - iv) Draw the resultant circuit (2marks)
- c) Draw a circuit that is minimal and equivalent to the circuit below (show the processes). (3marks)



QUESTION 3 [20 MARKS]

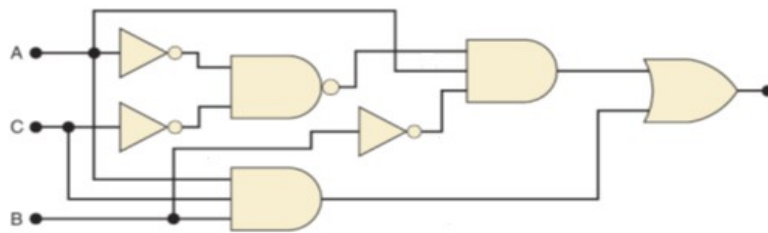- a) Draw the diagram and the truth table of an SR flip flop (4marks)
- b) Name FOUR computer ports, hence explain their functions in a digital computer (4marks)
- c) Below is un-minimised circuit. Use it to answer the questions below: -




- i) Simplify the above circuit (show the simplification process) (5marks)
 - ii) Draw a resultant circuit after the simplification. (2marks)
- d) With the help of a diagram, explain the process of recording data on a magnetic tape (5marks)

QUESTION 4 [20 MARKS]

- a) Design a simple circuit incorporating three LEDs, such that each one of the three LEDs lights when inputs 00, 01 and 11 respectively are applied on the circuit's inputs A and B. (Hint. show the truth table but do not minimize circuit) (4marks)
- b) Explain four basic types of registers found in a computer CPU (4marks)
- c) Explain THREE classification of combinational logic circuits, giving an example in each case. (6 marks)
- d) Using a Boolean logic example in each case, explain the following laws: -
 - i) Adsorption (2 marks)
 - ii) Consensus theorem (2 marks)
 - iii) Idempotent (2 marks)

QUESTION 5 [20 MARKS]

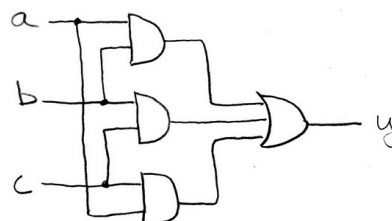- a) With the help of a Truth table, draw the circuit diagram and explain the working operation of a PIPO shift register. (9marks)
- b) Minimize the logic circuit below, and draw the minimised circuit (answer in POS) $Y = (A+B)(A+\bar{B}+C)(\bar{B}+C)$ (3 marks)
- c) Use the circuit below to answer the following questions



- i) Write output y in terms of a, b and c (2marks)
 - ii) Draw a truth table of the circuit above. (3marks)
 - iii) Draw electrical timing diagram of the resultant circuit (3marks)