

CHUKA



UNIVERSITY

UNIVERSITY EXAMINATIONS

CHUKA & EMBU

SECOND YEAR EXAMINATION FOR THE AWARD OF
DIPLOMA IN COMPUTER SCIENCE

COSC 0211: DIGITAL ELECTRONICS

STREAMS: DIP COMP.SCI (Y2S1)

TIME: 2 HOURS

DAY/DATE: FRIDAY 26/03/2021

2.30 P.M. – 4.30 P.M

INSTRUCTIONS:

- Answer question **ONE** and **TWO** other questions
- Do not write anything on the question paper
- This is a **closed book exam**, No reference materials are allowed in the examination room
- There will be **NO** use of mobile phones or any other unauthorized materials
- Write your answers legibly and use your time wisely.
- Marks are awarded for clear and concise answers.

SECTION A (ANSWER ALL QUESTIONS IN THIS SECTION)

QUESTION ONE (30 MARKS)

- a) By the aid of a diagram differentiate between a digital and analog signal [4 marks]
- b) Draw a logic circuit and truth table for $A + BC + C'$. [4 marks]
- c) Explain the De-Morgan Boolean law [2 marks]
- d) Derive the truth table for a two input NOR gate [2 marks]
- e) Sketch the standard symbols of the following basic logic gates and derive their truth tables.
 - i. OR gate [2 marks]
 - ii. AND gate [2 marks]
- f) Consider a three input NAND gate, the inputs are A, B, and C. Derive the truth table and draw the symbol for the expression. [4 marks]

COSC 0211

- g) Explain why NOR and NAND gate are referred to as universal gate [2 marks]
- h) Differentiate between RAM and ROM as used in memory [4 marks]
- i) Minimize $Y=(A+C).(AD+AD')+AC+C$ by use of Boolean laws [4 marks]

SECTION B (ANSWER ANY TWO QUESTIONS)

QUESTION TWO (20 MARKS)

- a) State two differences between combinational circuits and sequential circuits. [4 marks]
- b) Differentiate between a flip-flop and a latch [2 marks]
- c) By use of Boolean laws and rules minimize the following Boolean expressions (show your working)
- $Y=A'(A+B) + (B+AA)(A+B')$ [4 marks]
 - $Y=A'+AB$ [4 marks]
- d) Use NAND gate only to realize the following basic gates
- OR gate [3 marks]
 - AND gate [3 marks]

QUESTION THREE (20 MARKS)


- a) Differentiate between SOP and POS [4 marks]
- b) Consider the function below

$$F(A,B,C) = \sum m(2,4,5,6,7)$$

- Classify the above equation to either SOP or POS form and state why it belongs to that specific form [2 marks]
 - Construct the truth table for the equation [4 marks]
 - Draw the K-map of the equation [2 marks]
 - Minimize the equation using K-map [4 marks]
- c) Use only NOR gates to realize AND gate (show your working) [4 marks]

QUESTION FOUR (20 MARKS)

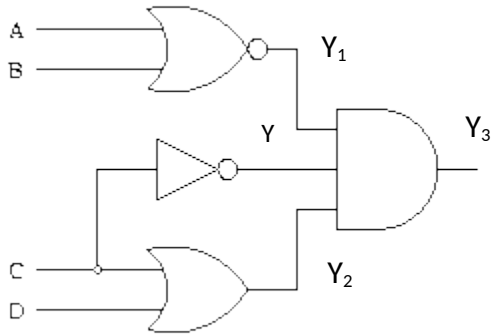a) Use the circuit below to answer the following questions



Derive the equation at:

Y [2 marks]

Y₁ [2 marks]

Y₂ [2 marks]

Y₃ [2 marks]

b) Discuss half adder illustrating its working, diagram and truth table [8 marks]

c) Discuss two types of ROM memory [4 marks]

QUESTION FIVE (20 MARKS)

a) Differentiate between SRAM and DRAM [4 marks]

b) Proof $A+A'B == A+B$ by use of

i. Boolean laws and rules [6 marks]

ii. Truth tables [4 marks]

c) Discuss the Boolean rules under the AND law [4 marks]

d) Discuss two clock triggering mechanisms [2 marks]
