

CHUKA



UNIVERSITY

UNIVERSITY EXAMINATIONS
THARAKA CAMPUS

SECOND YEAR EXAMINATION FOR THE AWARD OF CERTIFICATE IN COMPUTER
SCIENCE

COMP 00108: INTRODUCTION TO DIGITAL LOGIC AND DATA COMMUNICATION

STREAMS: CERT COMP SCI Y1S2

TIME: 2 HOURS

DAY/DATE: TUESDAY 3/12/2019
A.M - 1.30 P.M

11.30

INSTRUCTIONS :

- Answer question **ONE** and **TWO** other questions
- Do not write anything on the question paper
- This is a **closed book exam**, No reference materials are allowed in the examination room
- There will be **NO** use of mobile phones or any other unauthorized materials
- Write your answers legibly and use your time wisely.
- Marks are awarded for clear and concise answers.

QUESTION ONE (30 Marks)

- Using diagrams, briefly describe the **THREE** main data communication modes. (6 Marks)
- Describe the operation of the following gates while illustrating their symbols and the truth table.
 - AND gate (2 marks)
 - NOT gate (2 marks)
 - OR gate (2 marks)
 - XOR gate (2 marks)
- Distinguish between combinational and sequential circuits (4 marks)
- State two properties shared by all types of flip-flops (4 Marks)
- State and explain two types of parity checking in error detection (4 Marks)
- With the aid of diagrams, explain the operation of each type in **e)** above (4 Marks)

SECTION B (ANSWER ANY TWO QUESTIONS)

QUESTION TWO (20 MARKS)

a. Using well-labelled diagrams, explain the function of each of the following circuits:

a.i. Decoder (5 Marks)

a.ii. Multiplexer (5 Marks)

b. Draw a truth table and the logic gate implementation of the Boolean equation below:

(10 Marks)

$$F + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C}$$

QUESTION THREE (20 MARKS)

a. Illustrate the operation of each of the following flip-flops using their graphical symbols and truth tables:

a.i.i. S-R Flipflop (3 Marks)

a.i.ii. J-K Flipflop (3 Marks)

a.i.iii. D Flipflop (3 Marks)

b. Briefly describe the operation of a ripple counter. (5 Marks)

c. Draw each of the following for the ripple counter described in (b) above:

a.i.i. Sequential Circuit (3 Marks)

a.i.ii. Timing Diagram (3 Marks)

QUESTION FOUR (20 Marks)

a. Using NAND gates only, draw a logic gate implementation to realize the AND gate, OR gate and NOT Gate. (6 Marks)

b. Using NOR gates only, draw a logic gate implementation to realize the AND gate, OR gate and NOT Gate. (6 Marks)

c. Construct a truth table and draw the logic gate diagram for the following Boolean expressions:

i. $ABC + \overline{A}\overline{B}\overline{C}$
(4 Marks)

$ABC + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C}$ ii. (4
Marks)

QUESTION FIVE (20 Marks)

- a. Discuss the evolution of computers in terms of generations, stating and describing the technology used within each generation. (12 Marks)
- b. Briefly discuss each of the following as relates to error detection and correction (8 Marks)

a.i. Cyclic Redundancy Check

a.ii. Checksum

