

CHUKA



UNIVERSITY

## UNIVERSITY EXAMINATIONS

### THIRD YEAR EXAMINATION FOR THE AWARD OF DEGREE OF BACHELOR OF SCIENCE IN COMPUTER SCIENCE

#### COMP 304: COMPONENTS AND DESIGN TECHNIQUES FOR DIGITAL SYSTEMS

STREAMS:

TIME: 2 HOURS

DAY/DATE: WEDNESDAY 6/12/2017

8.30 A.M – 10.30 A.M

#### INSTRUCTIONS:

- Answer all questions in section A and any other two questions from section B.
- No Reference Material is allowed in the exam Room.
- All Mobile phones should be switched off in the exam room.


#### SECTION A (COMPULSORY)

#### QUESTION 1 (COMPULSORY) [30 MARKS]


- a) Using a TTL diagram, explain the operation of a NAND gate. (4marks)
- b) Using “*ieee.std\_logic\_1164.all*” library, write aVHDL program of a J-K flip flop. (5marks)
- c) With reference to counters, answer the following questions.
  - i. With the help of a digital circuit diagram, explain how a digital upwards counter functions (5marks)
  - ii. Draw the FSM diagram of the digital upward counter in (i) above (3marks)
- d) Use Karnaugh maps SOP to minimize the following circuit. (5 marks)

$$Z = \bar{A} + AB + \bar{A}\bar{B}C + A\bar{B} + C$$

 - e) Below is a digital circuit. Use it to answer the questions below: -



 - i) Simplify the above circuit (show the simplification process) (3marks)
- ii) Draw the simplified circuit using NAND gates only (2marks)
- iii) With the help of a diagram, illustrate how you would implement the simplified circuit using 7400 series IC shown below (3marks)



**SECTION B (Answer two question from this section)**


**QUESTION 2 [20 MARKS]**

a) A certain digital device could count number 1up to 16 in binary numbers. Draw a circuit which will enable this device give output of logic 1 only where there are three consecutive ones. i.e. 0111, 1110 etc. (9marks)

b) Use Demorgan theorem to prove that the following circuits are the same

i)  $A + A B = A$  (3marks)

ii)

 

(4marks)


- c) With regard to the principle of universality of NOR gates, using sketch diagrams, show how NOR gates could be used as: -
- i) AND gate
  - ii) NAND gate
- (4marks)

**QUESTION 3 [20 MARKS]**

- a) With reference to decoders
- i) Draw a circuit diagram of an 8 to 3 encoder using INVERTERS and gates only (4marks)
  - ii) Draw a truth table of the above encoder (4marks)
  - iii) Using “*ieee.std\_logic\_1164.all*” library, write a VHDL program of the decoder. (6marks)
- b) Using a diagram, explain the operation of a full adder (6marks)

**QUESTION 4 [20 MARKS]**

 - a) With the help of a digital circuit diagram, explain how a decimal to binary encoder functions (10marks)
- b) Below is a simple door open and lock FSM, explain how it functions and draw its state transition table (5marks)



- c) Explain the operation of an SR flip flop (5marks)

**QUESTION 5 [20 MARKS]**

- a) A certain student was tasked with designing a full adder which follows the following states

*Since the carry variable can either be 1 or 0. When the circuit is in the state where carry = 0, the relationship between the inputs A and B and the output S is such that: if AB = 00 then S = 0; if AB = 01 then S = 1; if AB = 10 then S = 1; and if AB = 11 then S = 0. When the circuit*

*is in the state where carry = 1, it also follows that: if  $AB = 00$  then  $S = 1$ ; if  $AB = 01$  then  $S = 0$ ; if  $AB = 10$  then  $S = 0$ ; and if  $AB = 11$  then  $S = 1$ .*

- i) Draw an FSM diagram of the above scenario (6marks)
- ii) Draw a state transition table of the above FSM (6 marks)

b) Using a Boolean, write an example of the following laws: -

- i) Dominance (2marks)
  - ii) Commutative (2marks)
  - iii) Idempotent (2marks)
  - iv) involution (2marks)
-