

CHUKA



UNIVERSITY

UNIVERSITY EXAMINATIONS

EXAMINATION FOR THE AWARD OF DEGREE OF BACHELOR OF SCIENCE IN
ELECTRICAL AND ELECTRONIC ENGINEERING

EENG 361: POWER SYSTEMS I

STREAMS: BSC EENG

TIME: 2 HOURS

DAY/DATE: THURSDAY 19/12/2024

11.30 P.M – 1.30 P.M.

INSTRUCTIONS:

Answer question ONE and any other TWO questions

Do not write on the question paper

QUESTION ONE (30 MARKS)

- Outline the merits of using per unit quantities in power systems analysis. [3 Marks]
- A three Phase generator with rating 1000KVA, 33KV has its armature resistance and synchronous reactance as $20\Omega/\text{Phase}$ and $70\Omega/\text{Phase}$. Calculate p.u. impedance of the generator. [3 Marks]
- Outline the advantages of GIS over conventional open air substations. [4 Marks]
- Draw the impedance diagram of the given SLD system in.

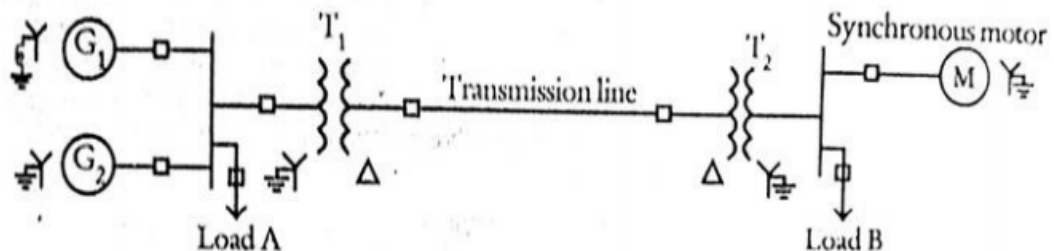


Fig 1 [4 Marks]

- e) Highlight the quantities specified and the quantities to be determined from load flow study for various types of buses. [4 Marks]
- f) Given $Z_0 = 0.199 \angle 90^0 pu, Z_1 = 0.175 \angle 90^0 pu, Z_2 = 0.175 \angle 90^0 pu$, compute the fault currents and voltages for a single line-to-ground fault. [6 Marks]
- g) Explain the structure of modern power system with neat sketch. [5 Marks]
- h) Define the term 'Flat start voltage' in load flow analysis. [1 Mark]

QUESTION TWO (20 MARKS)

- a) Draw the per unit impedance diagram for the power system shown in Fig.2. Neglect resistance and use a base of 100 MVA and 220 kV in 50 Ω line. The ratings of the generator, motor and transformers are:
 Generator : 40 MVA, 25 kV, X = 20%
 Motor : 50 MVA, 11 kV, X = 30%
 Y- Y Transformer: 40 MVA, 33/220 kV, X = 15%
 Y- Δ Transformer: 30 MVA, 220/11 kV, X = 15%.

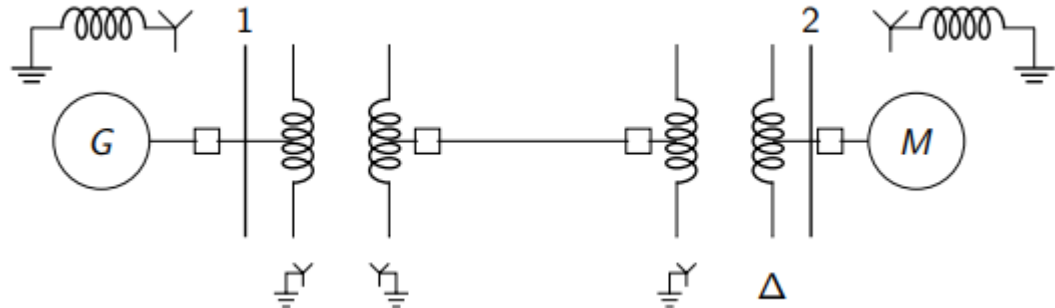


Fig.2

[10 Marks]

- b) Given $Z_0 = 0.199 \angle 90^0 pu, Z_1 = 0.175 \angle 90^0 pu, Z_2 = 0.175 \angle 90^0 pu$, compute the fault currents and voltages for a single line-to-ground fault. [6 Marks]
- c) Outline the assumptions made in short circuit studies [4 Marks]

QUESTION THREE (20 MARKS)

- a) For the network shown in Fig 3, form the bus admittance matrix. Determine the reduced admittance by eliminating node 4. The values are marked in p.u.

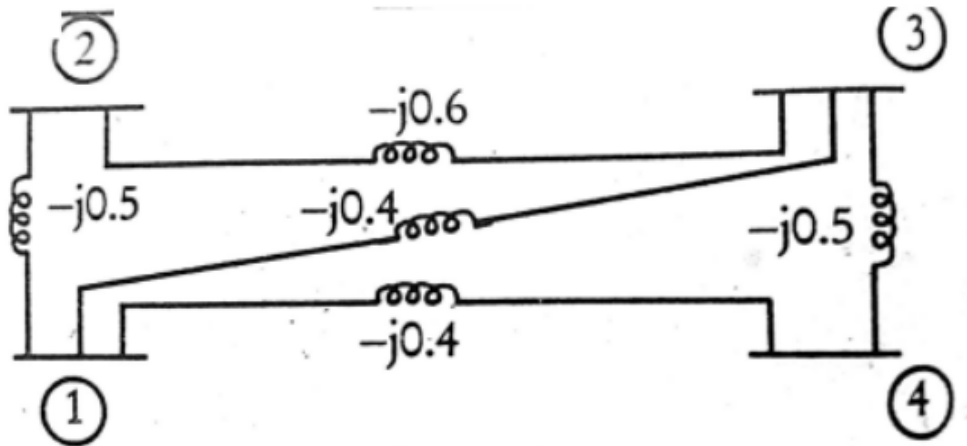


Fig.3

[10 Marks]

- b) Given $V_0 = 3.5 \angle 122^\circ$, $V_1 = 5.0 \angle -10^\circ$, $V_2 = 1.9 \angle 92^\circ$, find the phase sequence components. [6 Marks]
- c) Define Jacobian Matrix and outline how the elements of the Jacobian matrix are computed. [4 Marks]

QUESTION FOUR (20 MARKS)

- a) Figure 4 shows a three bus power system.
 Bus 1: Slack bus, $V=1.05 \angle 0^\circ$ p.u.
 Bus 2: PV bus, $|V|=1.0$ p.u., $P_g=3$ p.u.
 Bus 3: PQ bus, $P_L=4$ p.u., $Q_L=2$ p.u.

Carry out one iteration of load flow solution by Gauss seidel method. Neglect limits on reactive power generation.

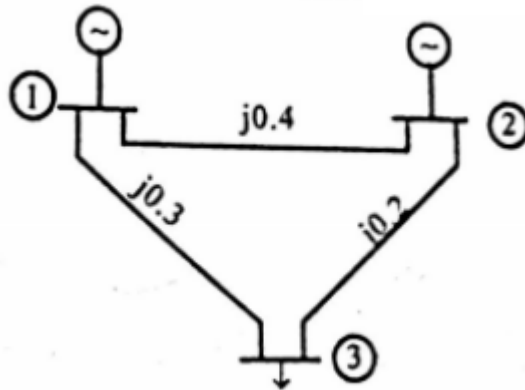


Fig.4 [14 Marks]

- a) Explain load flow analysis and give its significance in power systems analysis. [4 Marks]
- b) Highlight the disadvantages of Newton-Rhaphson method of load flow analysis and explain how they are overcome. [6 Marks]
-