

CHUKA

UNIVERSITY



UNIVERSITY EXAMINATIONS

**EXAMINATION FOR THE AWARD OF DEGREE OF BACHELOR OF SCIENCE
IN ELECTRICAL AND ELECTRONIC ENGINEERING**

EENG 455: ELECTRICAL NETWORK ANALYSIS**STREAMS: BSc. EENG****TIME: 2 HOURS****DAY/DATE: TUESDAY 09/04/2024****8.30 A.M. – 10.30 A.M.****INSTRUCTIONS**

- This examination paper contains **FOUR** questions.
 - Attempt **compulsory QUESTION ONE** and **any other TWO** questions.
- a. Define a PORT as used in electrical circuits and give examples of elements that makes a one port network (3 Marks)
 - b. Briefly explain what you understand by driving point impedance function (2 Marks)
 - c. Proof that the equivalent inductance for two parallel aiding inductors can be given by

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$
 (6 Marks)
 - d. Figure Q1 (d) below is a parallel connected source-free RLC network. find $v(t)$ if the initial conditions are $v_c(0) = 0$, $i_L(0) = -10A$. Sketch its corresponding $v(t)$ characteristic and comment on the type of damping in this case (7 Marks)

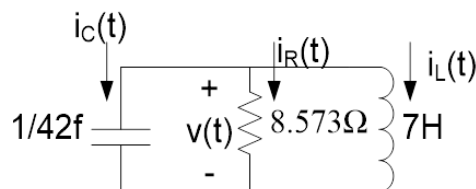


Figure Q1 (d)

- e. Find the transmission parameters for the circuit shown in figure Q1 (e) below (6 Marks)

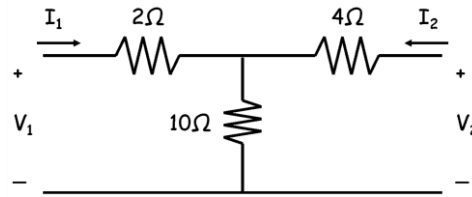


Figure Q1(e)

- f. The total inductance of two coils connected in series cumulatively is 1.6 H and connected differentially is 0.0.4 H. The self-inductance of one coil is 0.6 H. Calculate (6 Marks)
- (i) the mutual inductance and
 - (ii) the coupling coefficient.

QUESTION TWO (20 MARKS)

- a. (i) Define the term “Resonance” as used in electrical networks (1 Mark)
- (ii) Give three applications of resonance (3 Marks)
- b. Starting from basic principles, determine the y-parameters in terms of z-parameters. (7 Marks)
- c. Two inductors whose self-inductances are 75 mH and 55 mH respectively are connected in parallel aiding. Their mutual inductance is 22.5 mH. Calculate the effective inductance of the parallel combination. (3 Marks)
- d. Find the hybrid parameters for the two-port network shown in figure Q2 (d) below. (6 Marks)

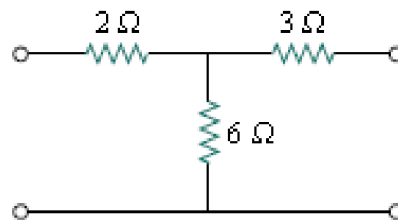


Figure Q2 (d)

QUESTION THREE (20 MARKS)

- a. Define the term “Bandwidth” (1 Mark)
- b. Explain what you understand by coefficient of coupling and give two of its properties (3 Marks)
- c. Show that the condition for symmetry for z-parameters can be given as $Z_{11}=Z_{22}$ (5 Marks)

- d. A circuit having a resistance of 4.0Ω with an inductance of 0.5 H and variable capacitance in series is connected across a 100 V , 50 Hz supply. Calculate: (6 Marks)
- The capacitance required to attain resonance
 - Voltage across the inductance and the capacitance at resonance
 - The Q factor of the circuit
- e. Two inductive coupled coils have self-inductance of $L_1=50\text{ mH}$ and $L_2=200\text{ mH}$. The coupling coefficient is 0.5 . (5 Marks)
- Find the mutual inductance
 - The maximum possible value of M

QUESTION FOUR (20 MARKS)

- Explain the term Dynamic impedance (1 Mark)
- What is the dynamic impedance for an ideal tank circuit with $R_s=0$ shown the figure Q4 (b) below (2 Marks)

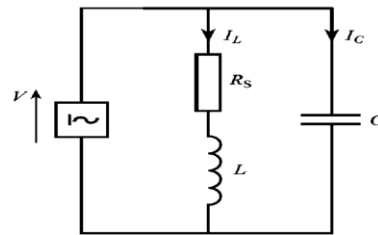


Figure Q4 (b)

- Starting from basic principles, show that the condition for transmission lines is $A=D$ (6 Marks)
- In the parallel RLC circuit shown in figure Q4 (d) below, $R=8\text{ k}\Omega$, $L=0.2\text{ mH}$ and $C=8\text{ }\mu\text{F}$. (6 Marks)
 - Calculate ω_r , Q and BW
 - Find ω_1 and ω_2
 - Determine the power dissipated at ω_r , ω_1 and ω_2

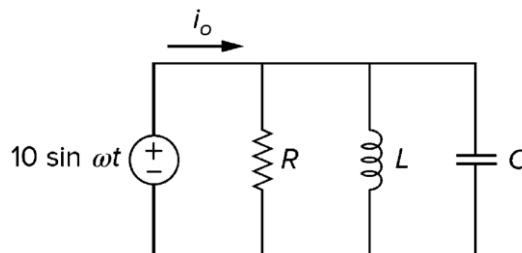


Figure Q4 (d)

- Find the Y-parameters of the circuit shown in figure Q4 (e) below. (5 Marks)

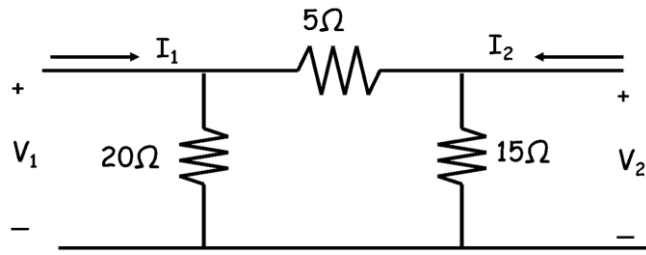


Figure Q4 (e)
